

# 实验 08 信号处理及有限状态机

## 实验目的

- 进一步熟悉 FPGA 开发的整体流程
- 掌握几种常见的信号处理技巧
- 掌握有限状态机的设计方法
- 能够使用有限状态机设计功能电路

## 实验环境

- VLAB: vlab.ustc.edu.cn
- FPGAOL: fpgaol.ustc.edu.cn
- Logisim
- Vivado


## 实验题目

题目 1. 在不改变电路功能和行为的前提下，将前面 Step5 中的代码改写成三段式有限状态机的形式，写出完整的 Verilog 代码。


代码如下：

```
module t1 (
    input clk,rst,
    output led
);
    reg [1:0] cnt;
    reg [1:0] cntnextstate;
    always@(*)
    begin
        cntnextstate=cnt+2'b1;
    end
    always@(posedge clk or posedge rst)
    begin
        if(rst)cnt<=2'b0;
        else cnt<=cntnextstate;
    end
    assign led=(cnt==2'b11)?1'b1:1'b0;
endmodule
```

 题目 2. 请在 Logisim 中设计一个 4bit 位宽的计数器电路，如下图所示，clk 信号为计数器时钟，复位时（rst==1）计数值为 0，在输入信号 sw 电平发生变化时，计数值 cnt 加 1，即在 sw 信号上升沿时刻和下降沿时刻各触发一次计数操作，其余时刻计数器保持不变。



按照实验文档说明中已经给出了取信号边沿（上升沿为例）得到一个周期的脉冲信号的技巧，对输入信号取反，再应用该技巧，即可得到上升沿和下降沿两个脉冲信号。两个信号或后即可得到状态转换的输入信号。据此原理，即可得到最终设计的电路图：

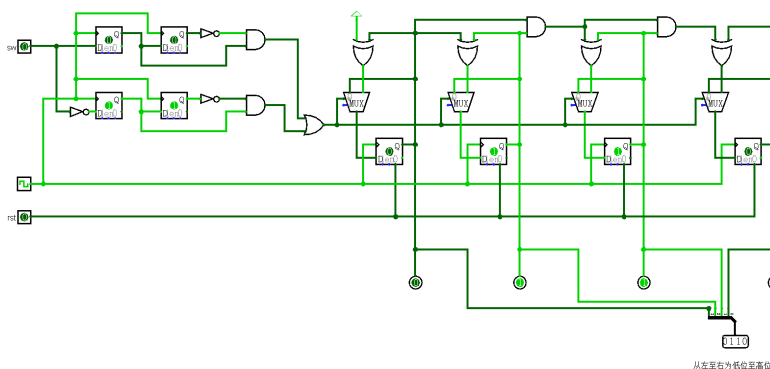

题目 3. 设计一个 8 位的十六进制计数器，时钟采用板载的 100MHz 时钟，通过 sw[0]控制计数模式，开关为 1 时为累加模式，为 0 时为递减模式，按键控制计数，按下的瞬间根据开关的状态进行累加或递减计数。计数值用数码管显示，其复位值为“1F”。

verilog 代码：

```
module counter (
    input clk,button,
    input [2:0] sw,
    output reg [3:0] out,
    output reg [2:0] selsct
);
    wire clk_n;
    wire button_n;
    wire button_edge;
    reg enable;
    reg [7:0] result;
    //信号处理
    jtrclr clr(.clk(clk),.button(button),.button_n(button_n));
    signal_edge cedge(.clk(clk),.button(button_n),.button_edge(button_edge)
    clk_wiz_0 clk_wiz_0_insr(.clk_in1(clk),.clk_out1(clk_n),.reset(sw[1]))
    //计数模块
```

```

always@(posedge clk or posedge sw[1])
begin
    if(sw[1])
    begin
        result<=8'h1f;
    end
    else
    begin
        if(button_edge)
        begin
            if(sw[0]) result<=result+8'b1;
            else result<=result-8'b1;
        end
    end
end
//输出信号选择模块
always@(posedge clk_n or posedge sw[1])
begin
    if(sw[1]) enable<=1'b0;
    else enable<=enable+1'b1;
end
always@(*)
begin
    case(enable)
    1'b0:begin selsct=3'b0; out=result[3:0]; end
    1'b1:begin selsct=3'b1; out=result[7:4]; end
    default:begin selsct=3'b0; out=result[3:0]; end
    endcase
end
endmodule

```

```

module jtrclr (//去毛刺
    input clk,button,
    output button_n
);
    reg [3:0] cnt;
    always@(posedge clk)
    begin
        if(button==1'b0) cnt<=4'h0;
        else if(cnt<4'h8)cnt<=cnt+4'b1;
    end
    assign button_n=cnt[3];
endmodule

```

```

module signal_edge(//取上升沿
    input clk,button,

    output button_edge

```

```
);
    reg button_r1,button_r2;
    always@(posedge clk)
    begin
        button_r1<=button;
    end
    always@(posedge clk)
    begin
        button_r2<=button_r1;
    end
    assign button_edge=button_r1&(~button_r2);
endmodule
```

需要用到的脚管约束文件如下：


```
set_property -dict { PACKAGE_PIN E3      IOSTANDARD LVCMOS33 } [get_ports {
set_property -dict { PACKAGE_PIN B18     IOSTANDARD LVCMOS33 } [get_ports {

set_property -dict { PACKAGE_PIN D14     IOSTANDARD LVCMOS33 } [get_ports {
set_property -dict { PACKAGE_PIN F16     IOSTANDARD LVCMOS33 } [get_ports {

set_property -dict { PACKAGE_PIN A14     IOSTANDARD LVCMOS33 } [get_ports {
set_property -dict { PACKAGE_PIN A13     IOSTANDARD LVCMOS33 } [get_ports {
set_property -dict { PACKAGE_PIN A16     IOSTANDARD LVCMOS33 } [get_ports {
set_property -dict { PACKAGE_PIN A15     IOSTANDARD LVCMOS33 } [get_ports {
set_property -dict { PACKAGE_PIN B17     IOSTANDARD LVCMOS33 } [get_ports {
set_property -dict { PACKAGE_PIN B16     IOSTANDARD LVCMOS33 } [get_ports {
set_property -dict { PACKAGE_PIN A18     IOSTANDARD LVCMOS33 } [get_ports {
```

题目 4. 使用有限状态机设计一个序列检测电路，并进行计数，当检测到输入序列为“1100”时，计数器加一，用一个数码管显示当前状态编码，一个数码管显示检测到目标序列的个数，用 4 个数码管显示最近输入的 4 个数值，用 sw[0]进行数据的串行输入，按键每按下一次将输入一次开关状态，时钟采用板载的 100MHz 时钟。要求画出状态跳转图，并在 FPGA 开发板上实现电路，例如当输入“0011001110011”时，目标序列个数应为 2，最近输入数值显“0011”，状态机编码则与具体实现有关。

由题意画出状态图如下 (Moore)：

 

有限状态机的 verilog 代码：

```

module statemachine(input clk,
                    input sw,
                    input btn,
                    output reg [2:0] hexplay_an,
                    output reg [3:0] hexplay_data);

    reg [2:0] curr_state;
    reg [2:0] next_state;

    // 取按钮边沿
    reg button_r1, button_r2;
    always@(posedge clk) button_r1 <= btn;
    always@(posedge clk) button_r2 <= button_r1;
    assign btn_pulse = button_r1 & (~button_r2);

    // 取状态边沿（因为是 Moore 型，需要取边沿来统计计数）
    reg state_r1, state_r2;
    always@(posedge clk) state_r1 <= curr_state[2];
    always@(posedge clk) state_r2 <= state_r1;
    assign state_pulse = state_r1 & (~state_r2);

    // 状态转换
    always(*) begin
        if (sw)
            case (curr_state)
                3'b000: next_state = 3'b001;
                3'b001: next_state = 3'b010;
                3'b010: next_state = 3'b010;
                3'b011: next_state = 3'b001;
                3'b100: next_state = 3'b001;
                default: next_state = 3'b000;
            endcase
        else
            case (curr_state)
                3'b010: next_state = 3'b011;
                3'b011: next_state = 3'b100;
                default: next_state = 3'b000;
            endcase
    end

```

```

        endcase
    end

    // 时序逻辑（检测按钮）
    reg [3:0] recent_num;
    always@(posedge clk) begin
        if (btn_pulse) begin
            curr_state    <= next_state;
            recent_num    <= recent_num << 1;
            recent_num[0] <= sw;
        end
        else begin
            curr_state <= curr_state;
            recent_num <= recent_num;
        end
    end
end

// 输出部分，需要输出 6 个数字，分时复用输出
reg [3:0] success_count;
always@(posedge clk) begin
    if (state_pulse) success_count <= success_count + 1;
    else success_count <= success_count;
end

reg [4:0] time_count;
always @(posedge clk) begin
    if (time_count == 5'b10111)
        time_count <= 5'b00000;
    else
        time_count <= time_count + 1;
end

always@(posedge clk) begin
    hexplay_an <= time_count[4:2];
    case (time_count[4:2])
        3'b000 : hexplay_data <= {1'b0, curr_state};
        3'b001 : hexplay_data <= success_count;
        3'b010 : hexplay_data <= {3'b000, recent_num[0]};
        3'b011 : hexplay_data <= {3'b000, recent_num[1]};
        3'b100 : hexplay_data <= {3'b000, recent_num[2]};
        3'b101 : hexplay_data <= {3'b000, recent_num[3]};
        default: hexplay_data <= 4'b0000;
    endcase
end
endmodule

```

脚管约束文件：

```

## This file is a general .xdc for FPGA0L_BOARD (adopted from Nexys4 DDR R
## To use it in a project:
## - uncomment the lines corresponding to used pins
## - rename the used ports (in each line, after get_ports) according to th

## Clock signal
set_property -dict { PACKAGE_PIN E3      IOSTANDARD LVCMOS33 } [get_ports {
create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_por
## FPGA0L BUTTON & SOFT_CLOCK
set_property -dict { PACKAGE_PIN B18     IOSTANDARD LVCMOS33 } [get_ports {
## FPGA0L LED (single-digit-SEGPLAY)
# set_property -dict { PACKAGE_PIN C17    IOSTANDARD LVCMOS33 } [get_ports
# set_property -dict { PACKAGE_PIN D18    IOSTANDARD LVCMOS33 } [get_ports
# set_property -dict { PACKAGE_PIN E18    IOSTANDARD LVCMOS33 } [get_ports
# set_property -dict { PACKAGE_PIN G17    IOSTANDARD LVCMOS33 } [get_ports
# set_property -dict { PACKAGE_PIN D17    IOSTANDARD LVCMOS33 } [get_ports
# set_property -dict { PACKAGE_PIN E17    IOSTANDARD LVCMOS33 } [get_ports
# set_property -dict { PACKAGE_PIN F18    IOSTANDARD LVCMOS33 } [get_ports
# set_property -dict { PACKAGE_PIN G18    IOSTANDARD LVCMOS33 } [get_ports

## FPGA0L SWITCH
set_property -dict { PACKAGE_PIN D14     IOSTANDARD LVCMOS33 } [get_ports {
set_property -dict { PACKAGE_PIN F16     IOSTANDARD LVCMOS33 } [get_ports {
# set_property -dict { PACKAGE_PIN G16    IOSTANDARD LVCMOS33 } [get_ports
# set_property -dict { PACKAGE_PIN H14    IOSTANDARD LVCMOS33 } [get_ports
# set_property -dict { PACKAGE_PIN E16    IOSTANDARD LVCMOS33 } [get_ports
# set_property -dict { PACKAGE_PIN F13    IOSTANDARD LVCMOS33 } [get_ports
# set_property -dict { PACKAGE_PIN G13    IOSTANDARD LVCMOS33 } [get_ports
# set_property -dict { PACKAGE_PIN H16    IOSTANDARD LVCMOS33 } [get_ports

## FPGA0L HEXPLAY

set_property -dict { PACKAGE_PIN A14     IOSTANDARD LVCMOS33 } [get_ports {
set_property -dict { PACKAGE_PIN A13     IOSTANDARD LVCMOS33 } [get_ports {
set_property -dict { PACKAGE_PIN A16     IOSTANDARD LVCMOS33 } [get_ports {
set_property -dict { PACKAGE_PIN A15     IOSTANDARD LVCMOS33 } [get_ports {
set_property -dict { PACKAGE_PIN B17     IOSTANDARD LVCMOS33 } [get_ports {
set_property -dict { PACKAGE_PIN B16     IOSTANDARD LVCMOS33 } [get_ports {
set_property -dict { PACKAGE_PIN A18     IOSTANDARD LVCMOS33 } [get_ports {

##USB-RS232 Interface

#set_property -dict { PACKAGE_PIN C4      IOSTANDARD LVCMOS33 } [get_ports {
#set_property -dict { PACKAGE_PIN D4      IOSTANDARD LVCMOS33 } [get_ports {
#set_property -dict { PACKAGE_PIN D3      IOSTANDARD LVCMOS33 } [get_ports {
#set_property -dict { PACKAGE_PIN E5      IOSTANDARD LVCMOS33 } [get_ports {

```

```
#set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets clk];  
#set_property CFGBVS VCC0 [current_design]  
#where value1 is either VCC0 or GND  
#set_property CONFIG_VOLTAGE 3.3 [current_design]  
#where value2 is the voltage provided to configuration bank 0
```

---

## 总结与思考

### 1. 请总结本次实验的收获

- 掌握了几种常用的数字信号处理技巧。
- 学习一种数字电路开发中非常重要的设计方法：有限状态机。
- 进一步巩固熟悉了使用 FPGA 进行数字电路设计开发全流程的各关键环节。

### 2. 请评价本次实验的难易程度

- 较难，需要学习信号整形及去毛刺，取信号边沿技巧等一系列很难的新知识，脑子要栈溢出了。

### 3. 请评价本次实验的任务量

- 接上条，较大。

### 4. 请为本次实验提供改进建议

- 实验渐进尾声，建议以后把学分提高（因为 1 学分和这个工作量真的不匹配啊），或者把实验练习与实验手册里的理论知识做分离，否则一周花费时间有点多。仅为个人建议。